
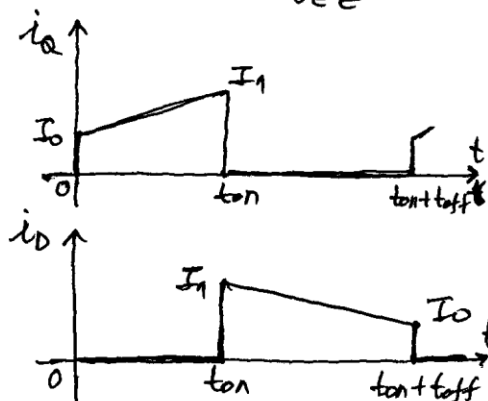


Na slici je prikazan Buck konvertor sa kolom za regulaciju napona na potrošaču. Upotrebljeni su idealni prekidači, operacioni pojačavač i komparator se napajaju iz baterija $V_{CC} = -V_{EE} = 12\text{ V}$, dok je: $L = 30\mu\text{H}$, $R_S = 10\text{ m}\Omega$, $R_1 C_1 \gg T_S$, a širina histerezisne petlje komparatora je

$V_H = 30\text{ mV}$. Smatrati da je talasnost napona na potrošaču zanemarljiva i da otpornost R_S ne utiče na rad konvertora. Odrediti i nacrtati, u ustaljenom stanju, vremenske dijagrame označenih napona, struja prekidača i induktivnosti kada je:

- $V_g = 12\text{ V}$ i $R = 0,5\Omega$,
- $V_g = 12\text{ V}$ i $R = 0,25\Omega$ i
- $V_g = 15\text{ V}$ i $R = 0,5\Omega$.

Rešenje:

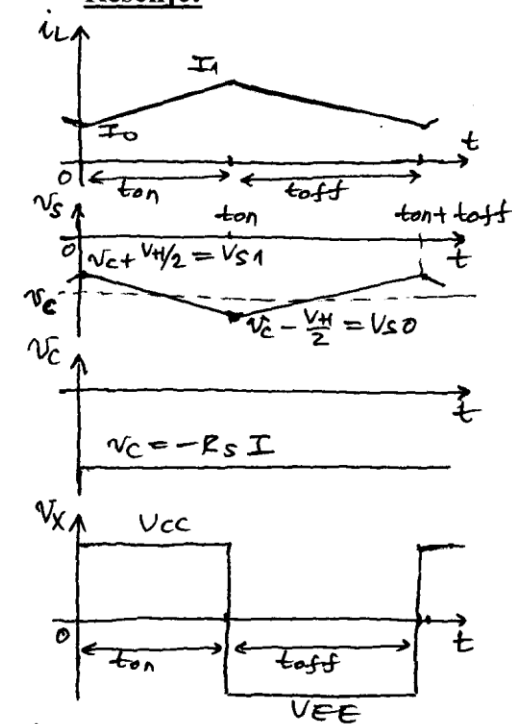

$$a) I_1 - I_0 = \frac{V_g - V}{L} t_{on} = \frac{V}{L} t_{off}$$

$$\frac{I_1 + I_0}{2} = \frac{V}{R} = \frac{V_{REF}}{R} = 10\text{ A}$$

$$I_1 - I_0 = \frac{V_H}{R_S} = 3\text{ A}$$

$$\frac{V_H}{R_S} = \frac{V_g - V}{L} t_{on} = \frac{V}{L} t_{off}$$

$$\Rightarrow T_S = t_{on} + t_{off} = \frac{V_H \cdot L}{R_S} \left[\frac{1}{V_g - V} + \frac{1}{V} \right] = 30,86\mu\text{S}$$

$$\Rightarrow t_{on} = 12,85\mu\text{S}, t_{off} = 18\mu\text{S} \text{ i } T_S = 30,85\mu\text{S}$$

$$D = \frac{t_{on}}{t_{on} + t_{off}} = 0,417, f_s = \frac{1}{T_S} \approx 32,4\text{ kHz}$$

$$V_C = -R_S \frac{I_1 + I_0}{2} = -R_S I = -100\text{ mV}$$

$$V_{S1} = V_C + \frac{V_H}{2} = -85\text{ mV}, V_{S0} = V_C - \frac{V_H}{2} = -115\text{ mV}$$

$$I_1 = I + \frac{V_H}{2R_S} = 11,5\text{ A}, I_0 = I - \frac{V_H}{2R_S} = 8,5\text{ A}.$$

$$b) V_g = 12\text{ V} \Rightarrow f_s \approx 32,4\text{ kHz}$$

$$V_C = -R_S I = -R_S \frac{V_{REF}}{R} = -200\text{ mV}$$

$$\Rightarrow V_{S1} = -185\text{ mV} \text{ i } V_{S0} = -215\text{ mV}$$

$$I_1 = I + \frac{V_H}{2R_S} = 21,5\text{ A}, I_0 = I - \frac{V_H}{2R_S} = 18,5\text{ A}.$$


$$c) T_S = \frac{V_H \cdot L}{R_S} \left[\frac{1}{V_g - V} + \frac{1}{V} \right] = 27\mu\text{S}$$

$$t_{on} = \frac{V_H}{R_S} \frac{L}{V_g - V} = 9\mu\text{S}, t_{off} = \frac{V_H}{R_S} \frac{L}{V} = 18\mu\text{S}$$

$$f_s = \frac{1}{T_S} \approx 37\text{ kHz}$$

$$V_C = -R_S \frac{V_{REF}}{R} = -100\text{ mV}$$
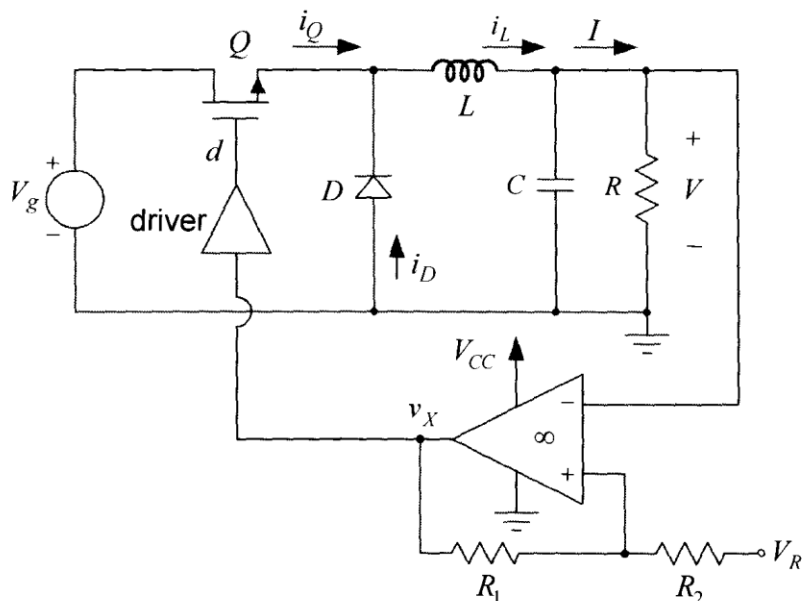
$$V_{S1} = -85\text{ mV} \text{ i } V_{S0} = -115\text{ mV}.$$



U buck konvertoru sa slike ulazni napon i potrošnja se menjaju u opsegu $15\text{V} \leq V_g \leq 25\text{V}$ i $2\text{A} \leq I \leq 5\text{A}$. Prekidački tranzistor i operacioni pojačavač se mogu smatrati idealnim, dok je $V_{CC} = 12\text{V}$, $V_D = 0,5\text{V}$, $L = 50\mu\text{H}$, $C = 100\mu\text{F}$ i $R_2 = 1\text{k}\Omega$.

- Odrediti otpornost R_1 i napon V_R tako da srednja vrednost izlaznog napona bude $V = 5\text{V}$, a talasnost $\Delta v_{p-p} = 1\%V$.
- Odrediti zavisnost prekidačke učestanosti konvertora u funkciji ulaznog napona

$f_s = f(V_g)$. Pri proračunu struje induktivnosti zanemariti talasnost izlaznog napona.

Rešenje:

a) operacioni pojačavač sa otpornostima R_1 i R_2 čini komparator sa histerezisom. Pragovi ovog komparatora su



$$V_1 = \frac{V_{CC}R_2 + V_R R_1}{R_1 + R_2} \quad \text{i} \quad V_2 = V_R \frac{R_1}{R_1 + R_2}$$

Izlazni napon se menja između ova dva praga

$$\Delta V_{p-p} = V_1 - V_2 = V_{CC} \frac{R_2}{R_1 + R_2} \Rightarrow R_1 = R_2 \left(\frac{V_{CC}}{\Delta V_{p-p}} - 1 \right) = 239\text{k}\Omega,$$

$$V = \frac{V_1 + V_2}{2} = \frac{1}{2} \frac{V_{CC}R_2 + 2V_R R_1}{R_1 + R_2} \Rightarrow V_R = V \left(1 + \frac{R_2}{R_1} \right) - \frac{V_{CC}}{2} \frac{R_2}{R_1}$$
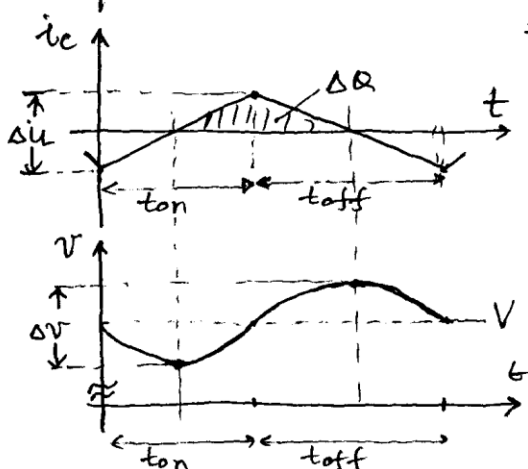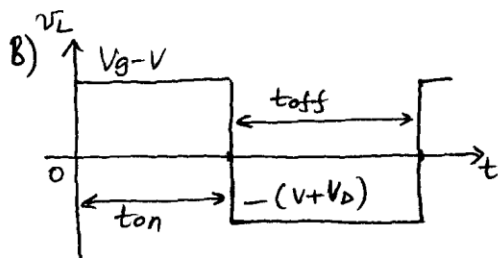
$$\Rightarrow V_R \approx V = 5\text{V}$$



$$V_{SB}: \bar{v}_L = 0 \Rightarrow (V_g - V)t_{on} - (V + V_D)t_{off} = 0$$

$$\Rightarrow V = (V_g + V_D) \frac{t_{on}}{T_s} - V_D \Rightarrow \frac{t_{on}}{T_s} = \frac{V + V_D}{V_g + V_D}$$

$$\Delta V = \frac{\Delta Q}{C} = \frac{1}{C} \cdot \frac{1}{2} \frac{\Delta i_L}{2} \left(\frac{t_{on}}{2} + \frac{t_{off}}{2} \right)$$

$$\Rightarrow \Delta V_{\xi} = \frac{\Delta i_L \cdot T_s}{8C}, \quad \Delta i_L = \frac{V + V_D}{L} \left(1 - \frac{t_{on}}{T_s} \right) T_s$$

$$\Rightarrow \Delta V_{\xi} = \frac{T_s^2}{8LC} (V + V_D) \left(1 - \frac{t_{on}}{T_s} \right)$$

$$\Rightarrow \Delta V_{\xi} = \frac{(V + V_D) \frac{V_g - V}{V_g + V_D}}{8LC f_s^2}$$

$$\Rightarrow f_s = \sqrt{\frac{1}{8LC \Delta V} \frac{(V_g - V)(V + V_D)}{V_g + V_D}}$$

$$f_s(V_g = 15\text{V}) = 42,12\text{kHz},$$

$$f_s(V_g = 25\text{V}) = 46,44\text{kHz}.$$