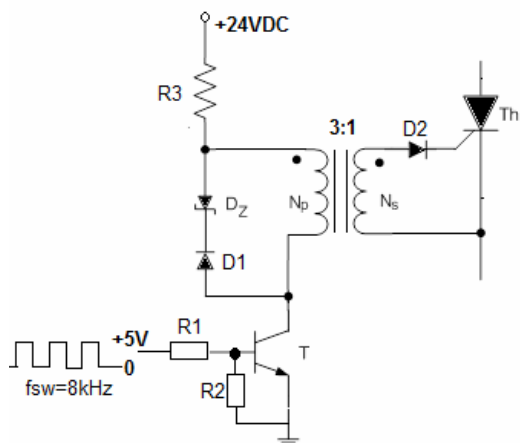


Usvojiti da je pad napona na diodama 0.6V, napon  $V_{bes}=0.75V$ , napon  $V_{ces}=0.2V$ , pojačanje tranzistora  $h_{fe}=400$ . Induktivnost magnećenja impulsnog transformatora je 100mH, dok je njegova rasipna induktivnost zanemarljiva.





# PRILOG ZA ZADATAK 01:

Tabela 1-Karakteristike tiristorskog modula SKKT460

| Symbol           | Conditions                                              | Values         | Units |
|------------------|---------------------------------------------------------|----------------|-------|
| $I_{TAV}$        | sin. 180; $T_c = 85$ (100) °C;                          | 460 (335)      | A     |
| $I_{TSM}$        | $T_{vj} = 25$ °C; 10 ms                                 | 18000          | A     |
|                  | $T_{vj} = 130$ °C; 10 ms                                | 15500          | A     |
| $i^2t$           | $T_{vj} = 25$ °C; 8,3 ... 10 ms                         | 1620000        | A²s   |
|                  | $T_{vj} = 130$ °C; 8,3 ... 10 ms                        | 1200000        | A²s   |
| $V_T$            | $T_{vj} = 25$ °C; $I_T = 1400$ A                        | max. 1,6       | V     |
| $V_{T(TO)}$      | $T_{vj} = 130$ °C                                       | max. 0,88      | V     |
| $r_T$            | $T_{vj} = 130$ °C                                       | max. 0,45      | mΩ    |
| $I_{DD}; I_{RD}$ | $T_{vj} = 130$ °C; $V_{RD} = V_{RRM}; V_{DD} = V_{DRM}$ | max. 240       | mA    |
| $t_{gd}$         | $T_{vj} = 25$ °C; $I_G = 1$ A; $di_G/dt = 1$ A/μs       | 1              | μs    |
| $t_{gr}$         | $V_D = 0,67 \cdot V_{DRM}$                              | 2              | μs    |
| $(di/dt)_{cr}$   | $T_{vj} = 130$ °C                                       | max. 250       | A/μs  |
| $(dv/dt)_{cr}$   | $T_{vj} = 130$ °C                                       | max. 1000      | V/μs  |
| $t_q$            | $T_{vj} = 130$ °C                                       | 100 ... 200    | μs    |
| $I_H$            | $T_{vj} = 25$ °C; typ. / max.                           | 150 / 500      | mA    |
| $I_L$            | $T_{vj} = 25$ °C; $R_G = 33$ Ω; typ. / max.             | 300 / 2000     | mA    |
| $V_{GT}$         | $T_{vj} = 25$ °C; d.c.                                  | min. 3         | V     |
| $I_{GT}$         | $T_{vj} = 25$ °C; d.c.                                  | min. 200       | mA    |
| $V_{GD}$         | $T_{vj} = 130$ °C; d.c.                                 | max. 0,25      | V     |
| $I_{GD}$         | $T_{vj} = 130$ °C; d.c.                                 | max. 10        | mA    |
| $R_{th(j-c)}$    | cont.; per thyristor / per module                       | 0,072 / 0,035  | K/W   |
| $R_{th(j-c)}$    | sin. 180°; per thyristor / per module                   | 0,074 / 0,037  | K/W   |
| $R_{th(j-c)}$    | rec. 120°; per thyristor / per module                   | 0,078 / 0,039  | K/W   |
| $R_{th(c-s)}$    | per thyristor / per module                              | 0,02 / 0,01    | K/W   |
| $T_{vj}$         |                                                         | - 40 ... + 130 | °C    |
| $T_{stg}$        |                                                         | - 40 ... + 125 | °C    |

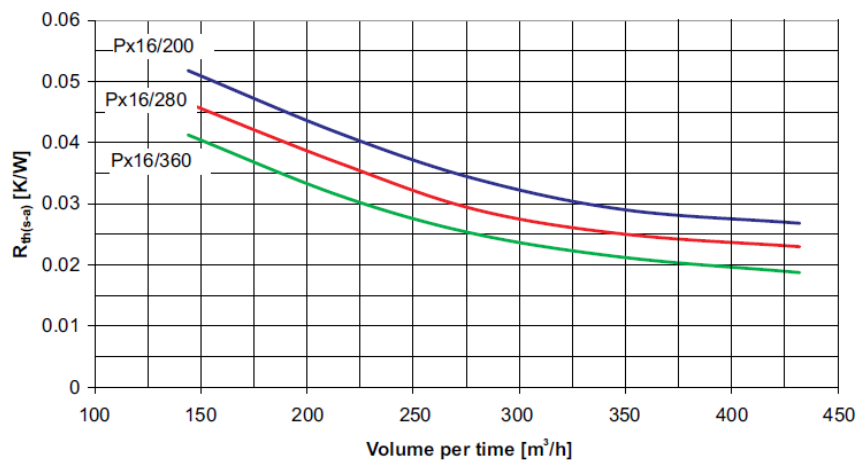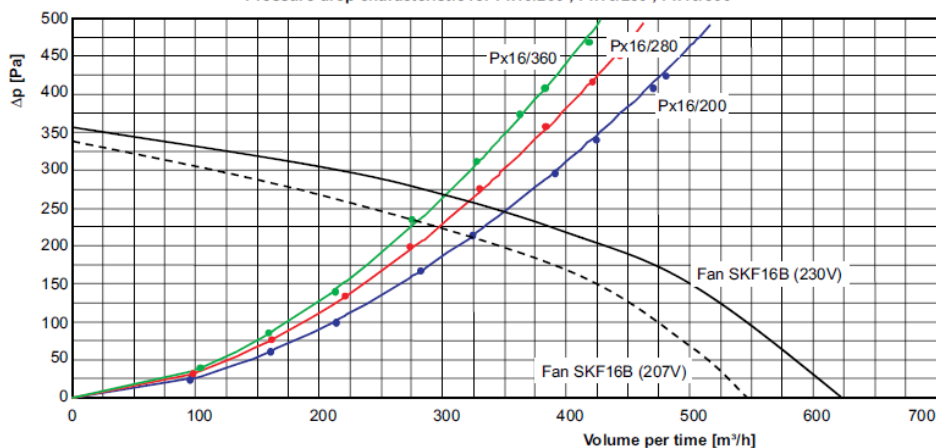
## Karakteristike hladnjaka i ventilatora

Pressure drop characteristic for Px16/200 ; Px16/280 ; Px16/360




1242515AL

(1)

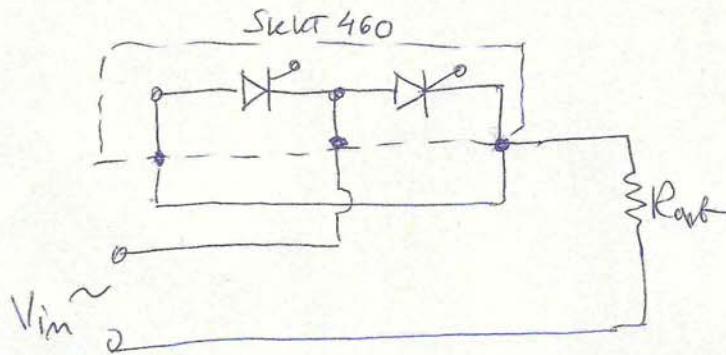

$$V_{in} = 400V \pm 10\% \\ 50/12$$

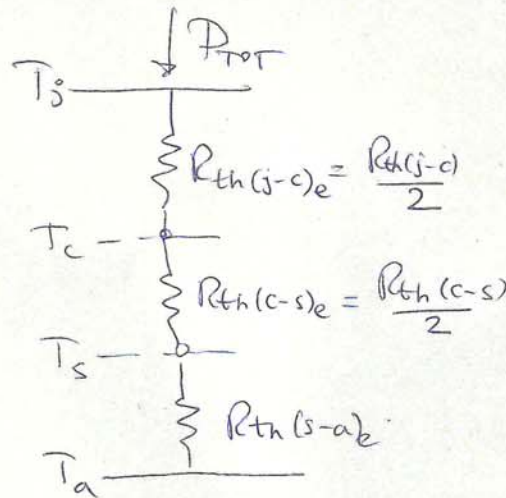

$$P_{tot} = \frac{T_j - T_a}{\Sigma R_{th}}$$

$$P_{tot} = \frac{T_j - T_a}{R_{th(j-c)} + R_{th(c-s)} + R_{th(s-a)}}$$

$$R_{th(j-c)} = \frac{9074}{2} = 9037 \frac{K}{W}$$

$$R_{th(c-s)} = \frac{902}{2} = 901 \frac{K}{W}$$

$$R_{th(s-a)} = ?$$

$$Z_A \text{ Henryk P16/200 Pri } 207V_n \rightarrow \text{propon } 325 \frac{m^3}{h}$$

$$Z_A 325 \frac{m^3}{h} \rightarrow R_{th(s-a)} = 0,03 \frac{K}{W}$$

$$P_{tot1} = \frac{100 - (-25)}{9037 + 901 + 903} = 1623,3 W = 1,62 kW$$

$$P_{tot2} = \frac{100 - 40}{9037 + 901 + 903} = 779,2 W \rightarrow 0,78 kW$$

$$\text{PO zgodnie } P_{tot1}^{(1)} = V_{T0} \frac{I_{m1}}{\pi} + r_d \frac{I_{m1}^2}{4} = \frac{P_{tot1}}{2} = 811,65 W$$

(2)

$$P_{tot1}^{(1)} = V_{T0} \cdot \frac{I_{m1}}{\pi} + r_d \frac{I_{m1}^2}{4} \cdot \frac{1}{r_d}$$

$$\frac{4}{r_d} \cdot P_{tot1}^{(1)} = \frac{4V_{T0}I_{m1}}{\pi r_d} + I_{m1}^2$$

12. case 1:

$$V_{T0} = 0,9$$

$$r_d = 0,45 \text{ m}\Omega$$

$$P_{tot1}^{(1)} = 811,65 \text{ W}$$

$$I_{m1} = -\frac{2V_{T0}}{\pi r_d} \pm \sqrt{\frac{4V_{T0}^2}{(\pi r_d)^2} + \frac{16P_{tot1}^{(1)}}{4r_d}}$$

$$I_{m1} = -\frac{2 \cdot 0,9 \cdot 10^3}{\pi \cdot 0,45} \pm \sqrt{\frac{4 \cdot (0,9)^2}{(\pi \cdot 0,45)^2} \cdot 10^6 + \frac{16 \cdot 811,65}{4 \cdot 0,45} \cdot 10^3}$$

$$= -1,274 \cdot 10^3 \pm \sqrt{1,6228 \cdot 10^6 + 7,214 \cdot 10^6}$$

$$= -1,274 \cdot 10^3 \pm 2,973 \cdot 10^3 \Rightarrow I_{m1} = 16994$$

Efektivni meanat snage opterećen:

$$= 1700 \text{ A}$$

$$I_{eff, opt1} = \frac{1700}{\sqrt{2}} = 1200 \text{ A}$$

$$I_{TAV} = \frac{I_{m1}}{\pi} = 540 \text{ A} > \begin{cases} I_{TAV, doz.} = 460 \text{ A NA} + 80^\circ\text{C} \\ = 335 \text{ A NA} + 100^\circ\text{C} \end{cases} \quad \begin{matrix} \text{u tabeli 1 za IGBT} \\ \text{Dov.} \\ \text{vrednosti} \end{matrix}$$

$$S_{opt} = \frac{\pi \cdot 335 \text{ A} \cdot 440 \text{ V}}{\sqrt{2}} = 327,2 \text{ kW}$$

$$I_{eff, opt}^* = 1200 \text{ A} \rightarrow P_{tot1}^* = V_{T0} \cdot \frac{I_{m1}^*}{\pi} + r_d \frac{I_{m1}^{*2}}{4} = 0,9 \cdot 335 \cdot \pi + 0,45 \text{ m}\Omega \cdot \frac{(335 \cdot \pi)^2}{4} = 1079 \text{ W}$$

$$T_{\Sigma} = R_{th(s-a)} \cdot P_{tot1}^* + T_{a1} = 0,03 \cdot 1079 + (-25^\circ\text{C}) = 7,13^\circ\text{C}$$

$$* \text{ za } I_{TAV} = 460 \text{ A } I_{m1} = \pi \cdot 460 = 1450 \text{ A} \Rightarrow I_{eff} = \frac{I_{m1}}{\sqrt{2}} = 1024 \text{ A}$$

$$I_{eff, opt} = 1024 \text{ A} \rightarrow S_{opt} = 1024 \cdot 440 = 450 \text{ kW}$$

$$* \text{ za } I_{TAV} = 540 \text{ A } I_{m1} = \pi \cdot 540 = 1696 \text{ A} \Rightarrow I_{eff} = \frac{I_{m1}}{\sqrt{2}} = 1200 \text{ A}$$

$$I_{eff, opt} = 1200 \text{ A} \rightarrow S_{opt} = 1200 \cdot 440 = 530 \text{ kW}$$



$$P_{tot2}^{(1)} = \frac{P_{tot2}}{2} = \frac{780}{2} = 390 \text{ W}$$

$$P_{tot2}^{(1)} = V_{to} \frac{I_{m2}}{\pi} + r_d \frac{I_{m2}^2}{4} \quad I_{m2} = \frac{2V_{to}}{\pi r_d} \pm \sqrt{\frac{4V_{to}^2}{(\pi r_d)^2} + \frac{16P_{tot2}^{(1)}}{4r_d}}$$

$$I_{m2} = -\frac{2 \cdot 0,9}{\pi \cdot 0,45} \cdot 10^3 \pm \sqrt{\frac{4 \cdot (0,9)^2}{(\pi \cdot 0,45)^2} \cdot 10^6 + \frac{16 \cdot 390}{4 \cdot 0,45} \cdot 10^3}$$

$$I_{m2} = -1,274 \cdot 10^3 \pm \sqrt{1,628 \cdot 10^6 + 3,466 \cdot 10^6}$$

$$= -1,274 \cdot 10^3 \pm 2,255 \cdot 10^3$$

$$I_{m2} = 9,182 \text{ uA} \approx 982 \text{ A}$$

$$I_{effopt2} = \frac{I_{m2}}{\sqrt{2}} = \frac{982}{1,41} = 696 \text{ A}$$

$$I_{TN} = \frac{I_{m2}}{\pi} = \underline{312 \text{ A}}$$

$$S_{opt} = 696 \text{ A} \cdot 440 \text{ V} = 306,2 \text{ kW}$$

Temp. ~~transistor~~ ~~in~~ ~~over~~ ~~from~~

$$T_{s2} = R_{th(s-a)} \cdot P_{tot2} + T_{a2}$$

$$= 0,03 \frac{\text{W}}{\text{W}} \cdot 780 \text{ W} + 40^\circ \text{C}$$

$$= 63,4^\circ \text{C}$$

$$23,6^\circ \text{C} \leq T_s \leq 63,4^\circ \text{C}$$

$$S_{max} = P_{max} = 320 \text{ W}$$

MAX. SWR  
noise  
in case of (R25)!

b)

④

$$\left. \frac{di_L}{dt} \right|_{t=0} = \frac{U_m}{L_u} \leq \frac{250 \text{ A}}{\mu\text{s}} \Rightarrow L_u \geq \frac{U_m}{250 \frac{\text{A}}{\mu\text{s}}}$$

$$U_m = 400 \cdot 1,1 \cdot \sqrt{2} = 620,4 \text{ V}$$

$$L_u \geq \frac{620,4}{250 \frac{\text{A}}{\mu\text{s}}} = 2,48 \mu\text{H} \rightarrow \underline{L_u = 3 \mu\text{H}}$$

$$\text{Zu } L_u^* = 3 \mu\text{H} \rightarrow \frac{di_L^*}{dt} = \frac{U_m}{L_u^*} = \frac{620,4 \text{ V}}{3 \mu\text{H}} = 206,8 \frac{\text{A}}{\mu\text{s}} < 250 \frac{\text{A}}{\mu\text{s}}$$

c)


$$T_{\text{SW}} = \frac{1}{f} = \frac{1}{8 \text{ kHz}} = 125 \mu\text{s}$$

$$V'' = V_{\text{ge}} + V_D = 3 + 0,6 = 3,6 \text{ V}$$

$$V' = \frac{N_I}{N_{II}} \cdot V'' = n \cdot V'' = 3 \cdot 3,6 = 10,8 \text{ V}$$

$$I'' = I_g = 1,5 \text{ A} \quad I' = \frac{I''}{3} = \frac{1,5}{3} = 0,5 \text{ A}$$
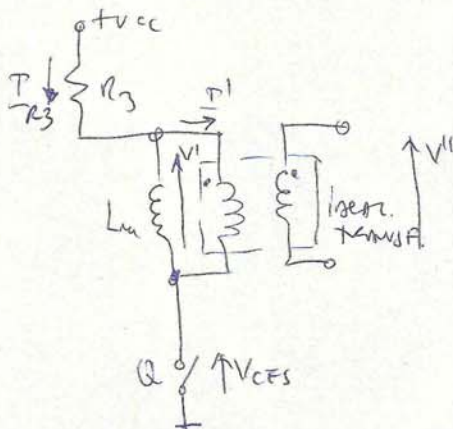
$$t_{\text{on}} = t_{\text{off}} \quad t_{\text{on}} + t_{\text{off}} = 2 \cdot 62,5 \mu\text{s} \Rightarrow t_{\text{on}} = t_{\text{off}} = \frac{1}{2} T = 62,5 \mu\text{s}$$




$$V_{\text{CC}} = R_3 I' + V' + V_{\text{CES}}$$

$$R_3 = \frac{V_{\text{CC}} - V' - V_{\text{CES}}}{I'} = \frac{24 - 10,8 - 0,2}{0,5} = 26 \Omega$$


$$I_{\text{eff}} = \frac{I'}{\sqrt{2}} = \frac{0,5}{1,41} = 0,35 \text{ A}$$

$$P_{R_3} = R_3 I_{\text{eff}}^2 = 26 \cdot 0,35^2 = 3,185 \text{ W}$$

$$R_3 = 27 \Omega / 5 \text{ W}$$

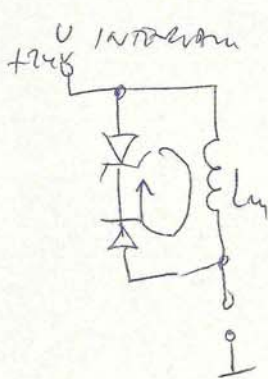

$t_{off} : i_L$

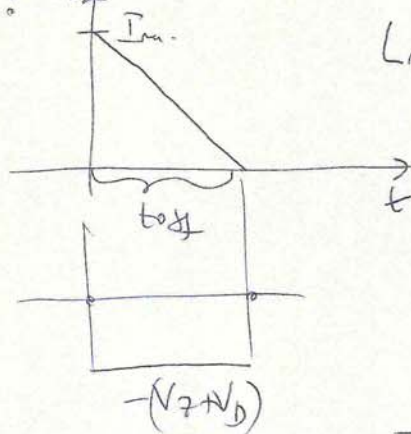


$$L_m \Delta i = V' t_{on}$$

$$\Delta i = I_m$$

$$I_m = \frac{V' t_{on}}{L_m}$$

$$I_m = \frac{10,5 \cdot 67,5 \mu s}{100 \cdot 10^{-3}}$$

$$I_m = 6,2 \text{ mA}$$

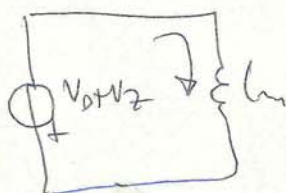

$$L_m \cdot \Delta i = (V_D + V_Z) t_{off}$$

$$t_{off} \leq 67,5 \mu s$$

$$t_{off} = \frac{L_m \Delta i}{V_D + V_Z} \leq 67,5 \mu s$$

$$V_D + V_Z \geq \frac{L_m \Delta i}{67,5 \mu s} = 11,7 \text{ V} \quad V_D = 0,6$$

$$V_Z = 11,7 - 0,6 = 10,5 \text{ V} \rightarrow V_Z^* = 11 \text{ V}$$

$$P_{DZ} = 11 \text{ V} \cdot 6,7 \text{ mA} = 0,737 \rightarrow 11 \text{ V} / 0,125 \text{ W}$$

$$\text{usando } R_2 = 100 \Omega$$

$$I_{R2} = \frac{V_{BE5}}{R_2} = \frac{0,75}{10 \cdot 10^{-3}} = 9,075 \text{ mA}$$

$$I_{C5} = I' = 9,5 \text{ A}$$


$$I_{BT} = \frac{9,5}{400} \Rightarrow I_{BT} = 1,25 \text{ mA}$$

$$I_{R1} = I_{BT} + I_{R2} = 9,075 \text{ mA} + 1,25 \text{ mA} = 1,325 \text{ mA}$$

$$V_{CC} = R_1 I_{R1} + V_{BE5} \Rightarrow R_1 = \frac{V_{CC} - V_{BE5}}{I_{R1}} = \frac{5 - 0,75}{1,325 \cdot 10^{-3}}$$

$$R_1 = 3,21 \text{ k}\Omega \rightarrow 3,3 \text{ k}\Omega$$

Proveito  $R_1$  i  $R_2$ :

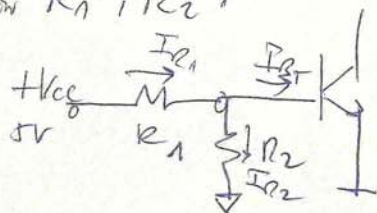



6

$$P_{R1} = R_1 I_{R1}^2 = 3,3 \cdot 10^3 \cdot 1,325^2 \cdot 10^{-6} = 6 \mu W$$


$$P_{R2} = R_2 I_{R2}^2 = 10 \cdot 10^3 \cdot 0,075^2 \cdot 10^{-6}$$

$$P_{R2} = 0,75 \mu W$$

$$R_1 = 3,3 k\Omega / 10 \mu W$$

$$R_2 = 10 k\Omega / 1 \mu W$$

$$R_3 = 270 \Omega / 5 W$$

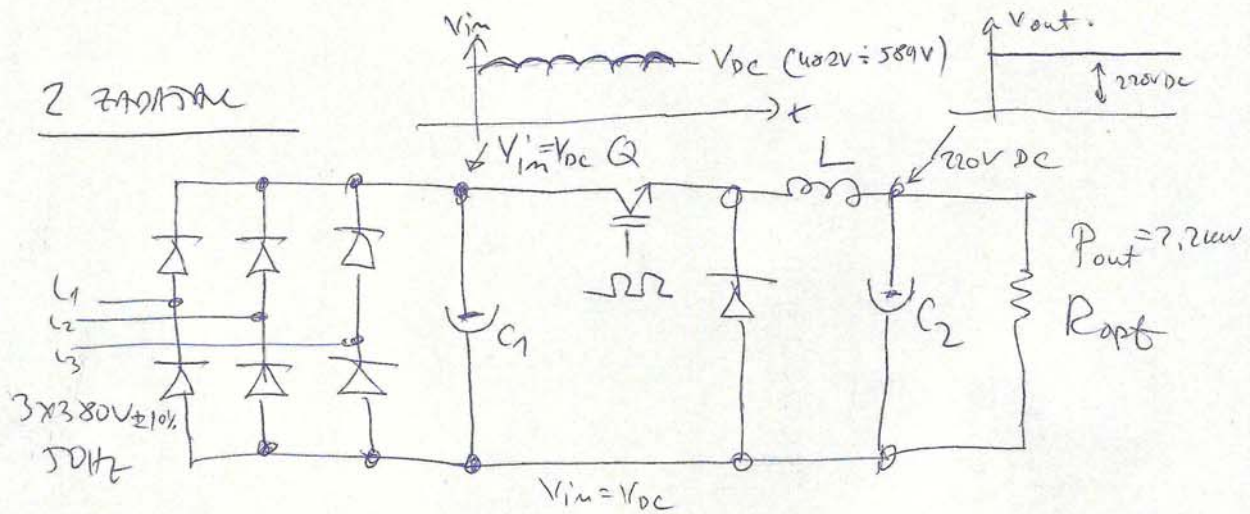

$$\frac{\Delta V_{in}}{V_{in}} = \frac{\Delta V_{in}}{V_{DC}} = 2 \cdot \frac{1}{12 f R_{eq} C - 1} \Rightarrow 12 f R_{eq} C - 1 = \frac{2}{\frac{\Delta V_{DC}}{V_{DC}}}$$

$$C_1 = \left( 1 + \frac{2 V_{DC}}{\Delta V_{DC}} \right) / 12 f R_{eq}$$

$$C_1 = \frac{1 + \frac{2 V_{DC}}{\Delta V_{DC}}}{12 f R_{eq}} = \frac{1 + \frac{2 V_{DC}}{\Delta V_{DC}}}{12 f \cdot \frac{V_{DC}}{I_{DC}}} = \frac{1 + \frac{2}{\frac{\Delta V_{DC}}{V_{DC}}}}{12 f \cdot \frac{V_{DC}}{I_{DC}}}$$

→ 5% (0,05)

$$C_1 \geq \frac{1 + \frac{2}{0,05}}{12 \cdot 50 \cdot \frac{500}{4,4}} = \frac{41}{68182} = 601,33 \mu F$$

ustawiamy  $C = 680 \mu F$ .  $V_{in} = V_{DC} \approx U_{eff_{max}} \cdot \sqrt{2}$

$$V_{in_{min}} = V_{DC_{min}} = (380 - 38) \sqrt{2} = 482,2 V$$

$$V_{in_{max}} = V_{DC_{max}} = (380 + 38) \sqrt{2} = 589,38 V$$

482,2 (V<sub>in</sub> = V<sub>DC</sub>) ≤ 589,38 V



$$482,2V \leq V_{in} \leq 589,38V$$

(7)

$$I_{Lsr} = I_{out} = \frac{220V}{22\Omega} = 10A$$

$$R_{opt} = \frac{V_{out}^2}{P} = \frac{220^2}{2200} = 22\Omega$$

$$\Delta i_L = \frac{\Delta i_L}{100} = \frac{10 \cdot 20}{100} = 2A$$

$$\delta_{min} \cdot V_{inmax} = 220$$

$$\delta_{min} = \frac{220}{589,38} = 0,373$$

$$\delta_{max} \cdot V_{inmin} = 220$$

$$\delta_{max} = \frac{220}{482,2} = 0,456$$

$$L \gg \frac{(V_{inmax} - V_{out}) \delta_{min}}{f_{sw} \cdot \Delta i_L}$$

$$L \gg \frac{589,38 - 220}{50 \cdot 10^3 \cdot 2} = 3,7 \mu H \rightarrow \underline{4 \mu H}$$

$$L^* = 4 \mu H$$

brojka se izmjenom minimiziran (482,2V) pri  $L^* = 4 \mu H$

$$\Delta i_L = \frac{V_{inmin} - V_{out}}{L^*} \cdot \frac{\delta_{max}}{f_{sw}} = \frac{(482,2 - 220) \cdot 0,456}{4 \cdot 10^{-3} \cdot 50 \cdot 10^3} = 0,59A$$

$$\Delta i_L < 2A$$

$$C_2 = \frac{1 - \delta_{min}}{8 \cdot L^* \cdot f_{sw}^2 \cdot \left( \frac{\partial V_{out}}{\partial V_{in}} \right)} = \frac{1 - 0,373}{8 \cdot 4 \cdot 10^{-3} \cdot 50^2 \cdot 10^6 \cdot 0,005} = \frac{0,627}{400000}$$

$0,5\% \Rightarrow 0,005$


$$C_2 = 1,567 \mu F \leftrightarrow \text{uzimamo } C_2 = \underline{2,2 \mu F} \text{ (uzetost se 50 kHz)}$$

$$\omega_{rez} = \frac{1}{\sqrt{L^* C_2^*}} = \frac{1}{\sqrt{4 \cdot 10^{-3} \cdot 2,2 \cdot 10^{-6}}} = 10660 \text{ rad/s}$$

$$f_{rez} = \frac{\omega_{rez}}{2\pi} = 1,697 \text{ kHz} \ll f_{sw} \text{ u}$$

Dioda mora da podnese I<sub>AV</sub> manje od 220V → manje diodama 400V  
 Neka gleda vrednost struje (MAX)  $(1 - \delta_{min}) \cdot I_{out} = (1 - 0,373) \cdot 10A = 6,27A$   
 uzimamo diodu D: 10A/400V, zatim I<sub>TSR</sub> = 0,456 · 10 = 4,56A → 10A  
 Doga se mogu izmjeniti na razliku 600V → manje traze 10A/1000V

3. 240 mW.

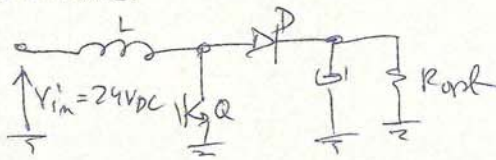

$$P_{out} = 300W$$

$$f_{sw} = 100 kHz \rightarrow T = 10 \mu s.$$

$$t_{off} = 5 \mu s \rightarrow t_{on} = 5 \mu s$$

$$\delta = \frac{t_{on}}{T} = \frac{1}{2}$$

$$V_{out} = \frac{V_{in}}{1 - \delta} = \frac{V_{in}}{1 - 0.5} = 2 V_{in} = 48V DC$$

$$R_{out} = \frac{48V}{I_{out}}$$

$$I_{out} = \frac{P_{out}}{V_{out}} = \frac{300}{48} = 6.25A$$

$$R_{out} = \frac{48}{6.25} = 7.68 \Omega$$

a)  $I_{DSR} = I_{out} = 6.25A$

b)  $V_{in} \cdot t_{on} = L \Delta i$

$$\frac{\Delta i}{I_{in}} \cdot 100 \leq 5 \Rightarrow \Delta i = \frac{5 I_{in}}{100}$$


$$I_{in} = \frac{300W}{24V} = 12.5A$$

$$\Delta i = \frac{5 \cdot 12.5}{100} = 0.625A$$

$$\frac{V_{in} \cdot t_{on}}{L} \leq 0.625A$$

$$L \geq \frac{V_{in} \cdot t_{on}}{0.625A} = \frac{24 \cdot 0.5 \cdot 10 \mu s}{0.625A}$$
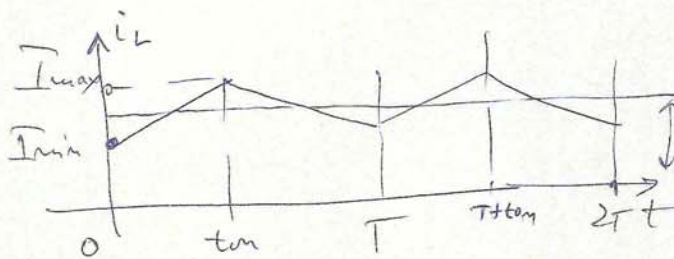
$$L \geq 192 \mu H \rightarrow \text{choose } L^* = 200 \mu H$$



$$I_{max} + I_{min} = 2 I_{in} = 25$$

$$I_{max} - I_{min} = 0.625$$

$$2 I_{max} = 25 + 0.625 \Rightarrow I_{max} = 12.8125A$$


$$I_{min} = I_{max} - \Delta i = 12.8125 - 0.625 = 12.1875A$$

|                                              |
|----------------------------------------------|
| $I_{max} = 12.8125A$<br>$I_{min} = 12.1875A$ |
|----------------------------------------------|



4 zadanje i

9

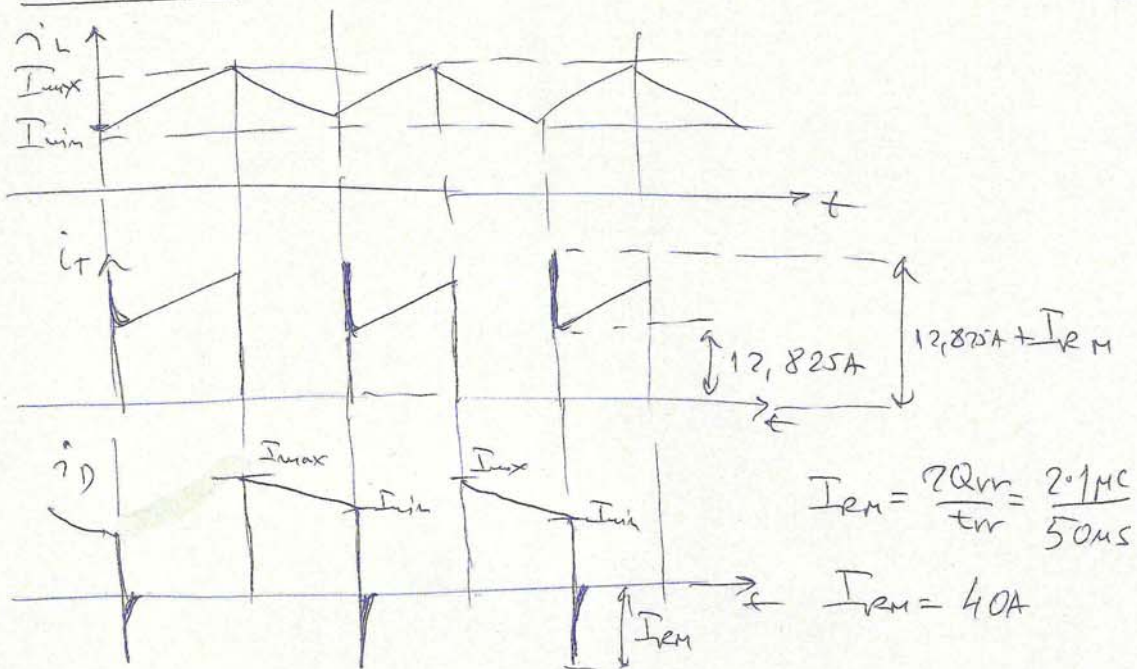


$I_{MAX \text{ trenutni sprot tranzistor}} = 12,825A + 40A = 52,825A \rightarrow \text{Bijemo LEM za } 100A$

Obično da je  $t_{err} = 50ns$ ,  $\frac{1}{t_{err}} \approx 20MHz \rightarrow \text{LEM za nepredvidljive veći prop. okrog } 100MHz$

$R_m \cdot \frac{100A}{5000} = 5V \Rightarrow R_m = 250\Omega$

Srednja vrednost  $\frac{100A}{5000} = 20mA$

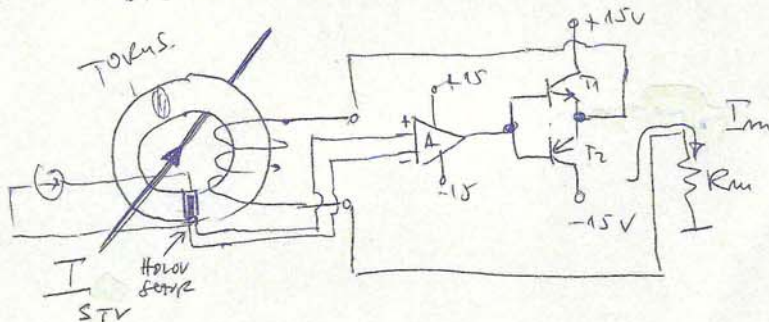$P_{dis} = R_m I_m^2 = 250 \cdot (0,02)^2 = 0,1W \Rightarrow \text{malo manje } 250\Omega / 0,25W$







*U Beogradu 30.01.2018-Predmetni profesor: Dr Željko Despotović, dipl.el.inž.*